
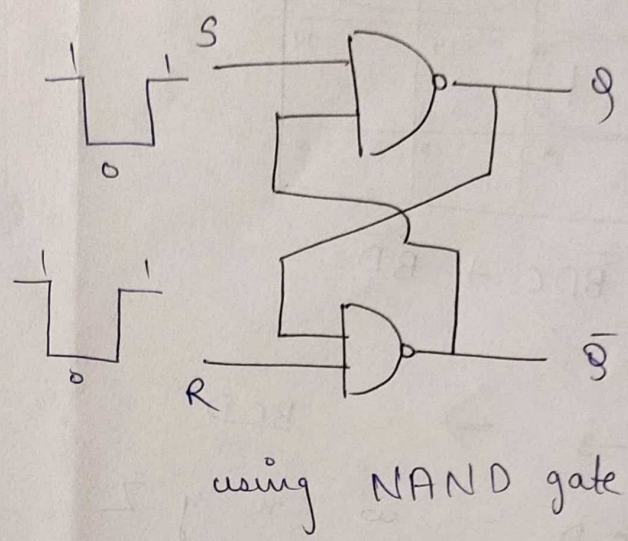


flip flops

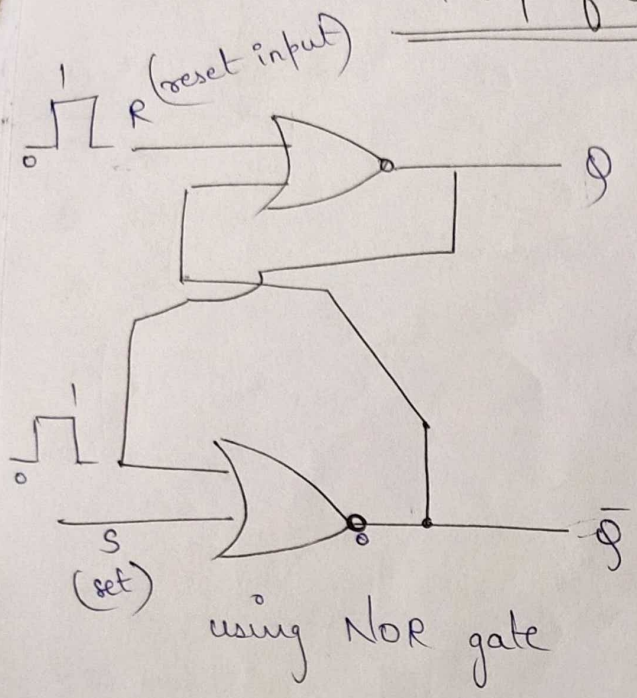

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

after $s=1; R=0$

after $s=0; R=1$

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

after $s=1; R=0$


after $s=0; R=1$

This provides a feedback path

~~Diff b/w flip~~

⇒ A flip flop circuit can maintain binary information indefinitely as long as the power is delivered to the circuit until directed by an input signal to switch state

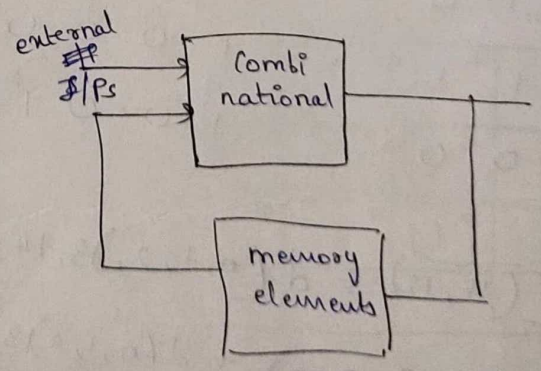⇒ basically it can be constructed using two NAND gates (or) NOR gates with cross coupled connection from o/p of one gate to i/p of other gate




flip flop is sequential c

Latch

- 1) o/p changes immediatly when I/p changes
- 2) It consumes less power because of simplex design and no clocking mechanism
- 3) Used in ~~more~~ mainly logical combinational circuits
- 4) no clock signal, gates used
- 5) Asynchronous sequential circuit

flip flop

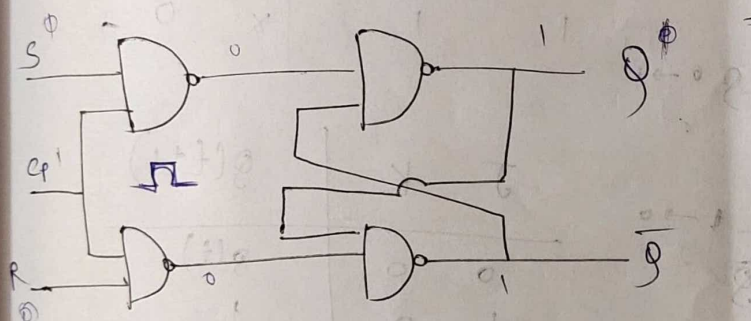- 1) o/p changes only with the clock signals
- 2) It consumes more power because of its ^{more complex} clocking mechanisms
- 3) Important modules in sequential circuits
- 4) Clock signal application is required
- 5) sequential ~~is~~ synchronous circuit




SR flip flop

Truth table


i/p's		o/p	
Q(t)	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

S	R	Q(t+1)
0	0	Q(t) ← no change
1	0	1 ← set the o/p to 1
0	1	0 ← reset the o/p to 0
1	1	xx invalid


⇒ characteristic equation

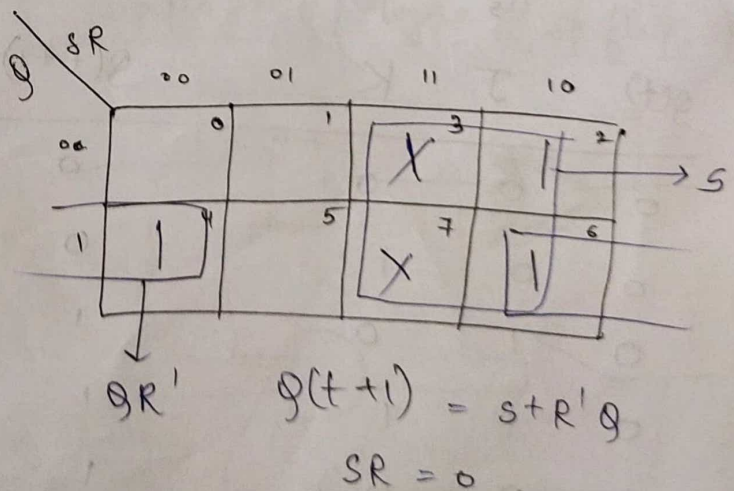

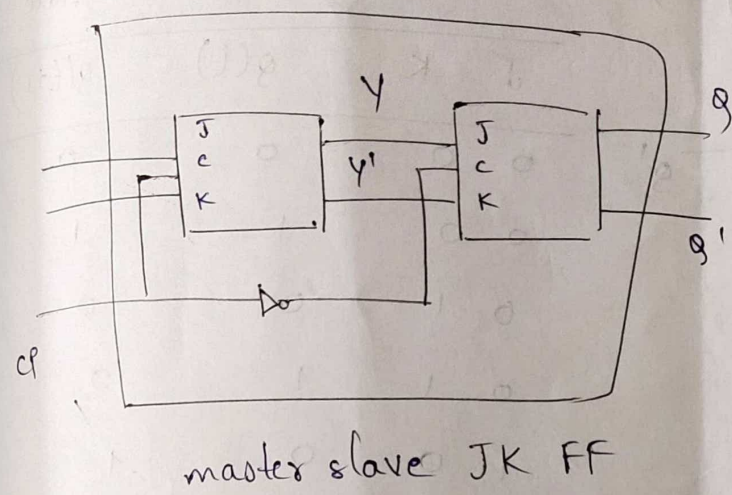
It can be avoided if $t_p < \Delta t$
 To avoid this situation
 master slave J-K flip flop can
 be used



master slave JK FF

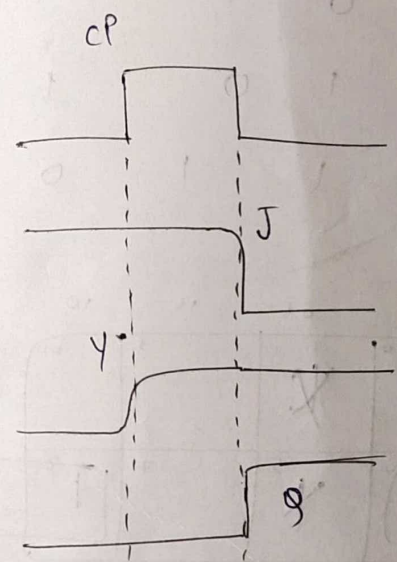


D-flip flop (Data flip flop)

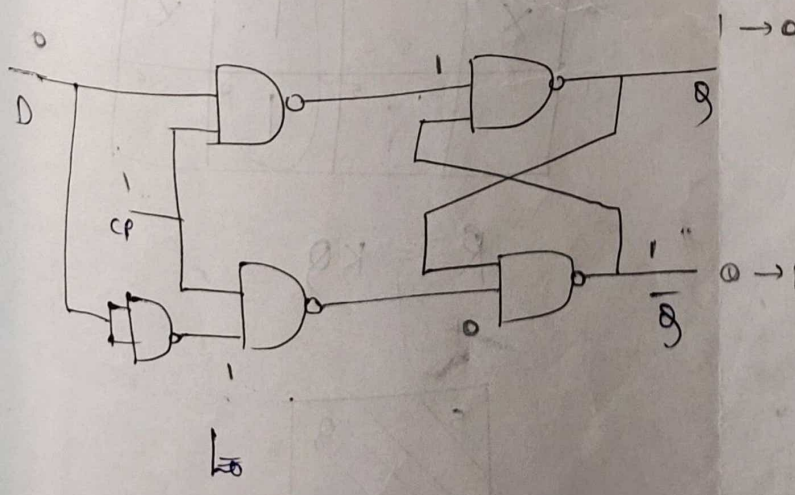

i/p _s		o/p	
Q(t)	D	Q(t+1)	
0	0	0	
0	1	1	
1	0	0	
1	1	1	

truth table

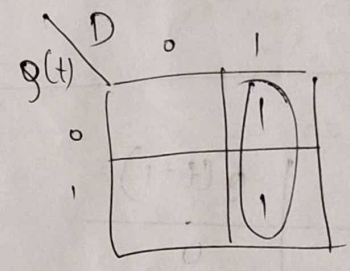


$Q(t+1) = D$
 characteristic equation


Excitation table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

T flip flop (Toggle flip flop)

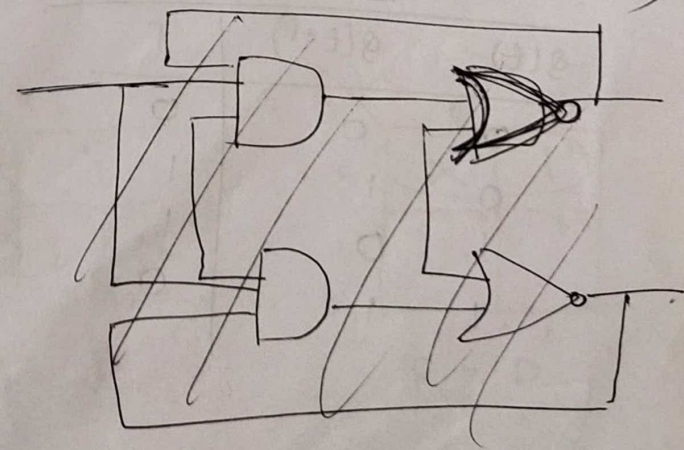

T flip flop

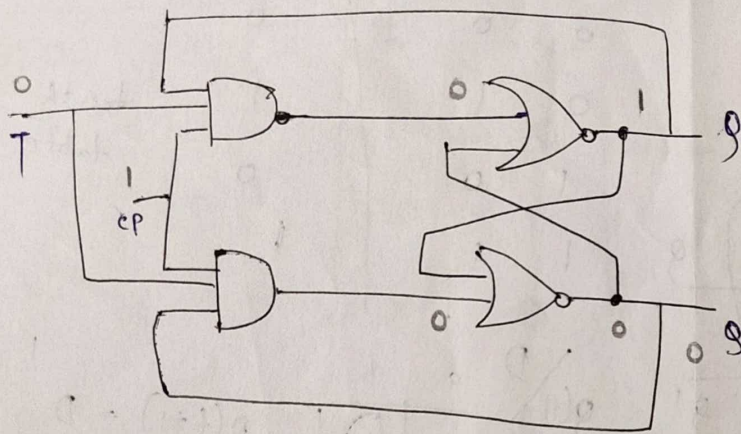

$Q(t)$	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

truth table

Q	T	0	1
0	0	0	1
1	0	1	1
1	1	1	0

$$Q(t+1) = TQ' + T'Q$$

characteristic eq


Excitation table

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0


flip-flop conversions

SR FF \rightarrow JK FF


	J	K	Present state $Q(t)$	Next state $Q(t+1)$
0	0	0	0	0
0	0	0	1	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	1
1	1	1	1	0

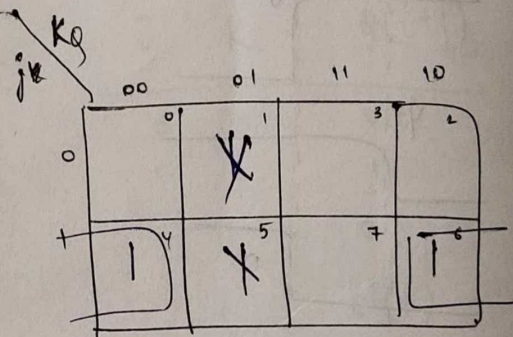

$$S = JQ'$$

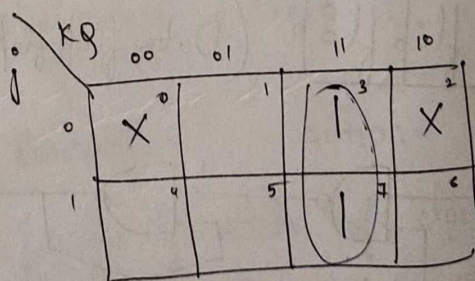

$$R = KQ$$

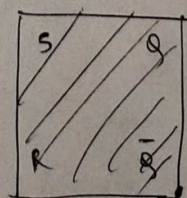

FF i/ps

S	R
0	x
x	0
0	x
0	1
1	0
x	0
1	0
0	1



i/ps		Present state	next state	FF i/ps	
S	R	Q(t)	Q(t+1)	J	K

0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


any other \rightarrow SR is not recommended as invalid

SR \rightarrow D


J	K	D	Q(t)	Q(t+1)	S	R
		0	0	0	0	x
		0	1	1	0	1
		1	0	0	1	0
		1	1	1	x	0

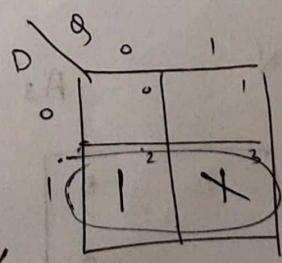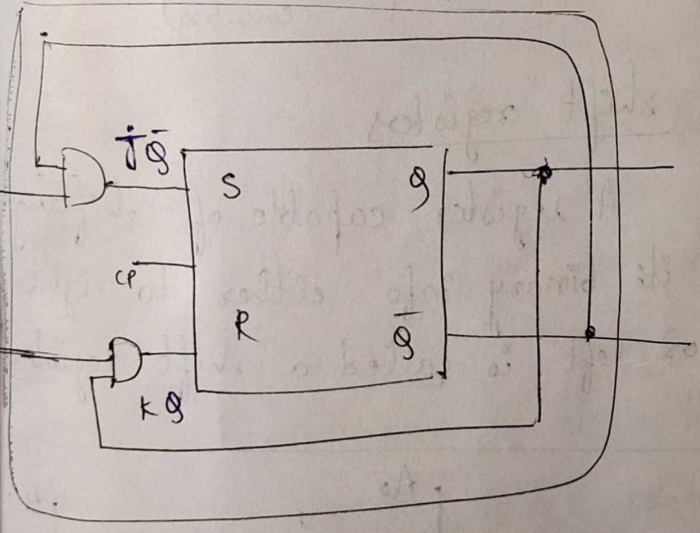

S = D

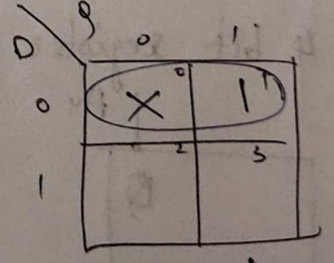

R = D'

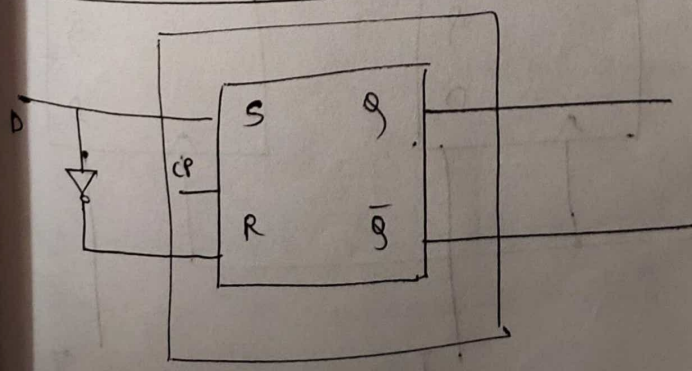

Assignment

Any two flip flop conversions

- T \rightarrow D
- D \rightarrow T